

# VLSI Design EE 523

## Spring 2024

**Shahid Masud**

**Lecture 21**

# Topics for lecture 21

---







- Dynamic Logic Circuits
- Cascading, Monotonicity
- Charge Sharing Problems
- Domino Circuit Design
- **Quiz 4 was held**

# DYNAMIC CMOS LOGIC

# What is Dynamic Logic?
    
## Dynamic Logic



- *Dynamic* gates use a clocked pMOS pullup
- Two modes: *precharge* and *evaluate*



# The FOOT Transistor

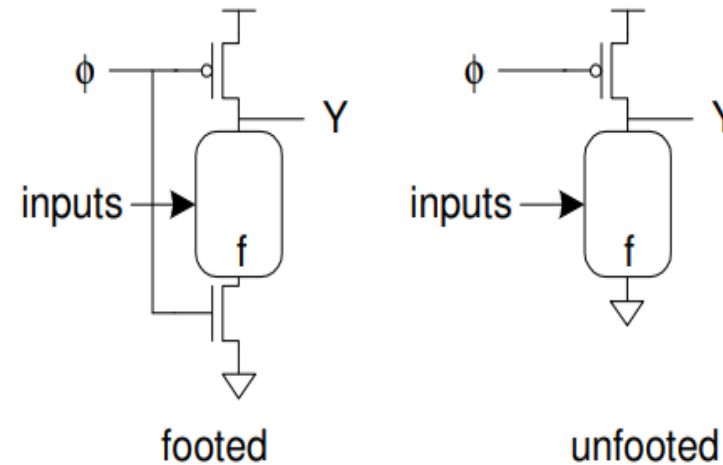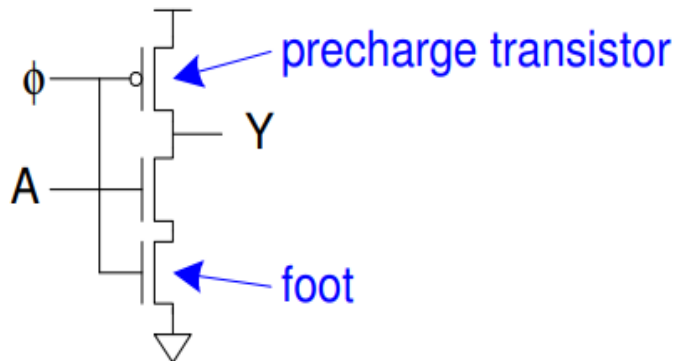
## The Foot

- What if pulldown network is ON during precharge?
- Use series evaluation transistor to prevent fight.



# Dynamic Logic Operation


## Dynamic Logic

 

$\Phi_n$  network


2 phase operation:

- Precharge
- Evaluation

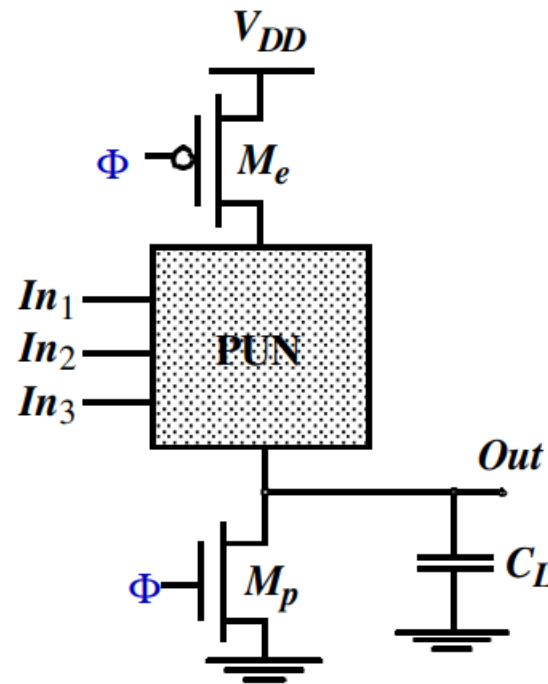


$\Phi_p$  network

## Logical Effort

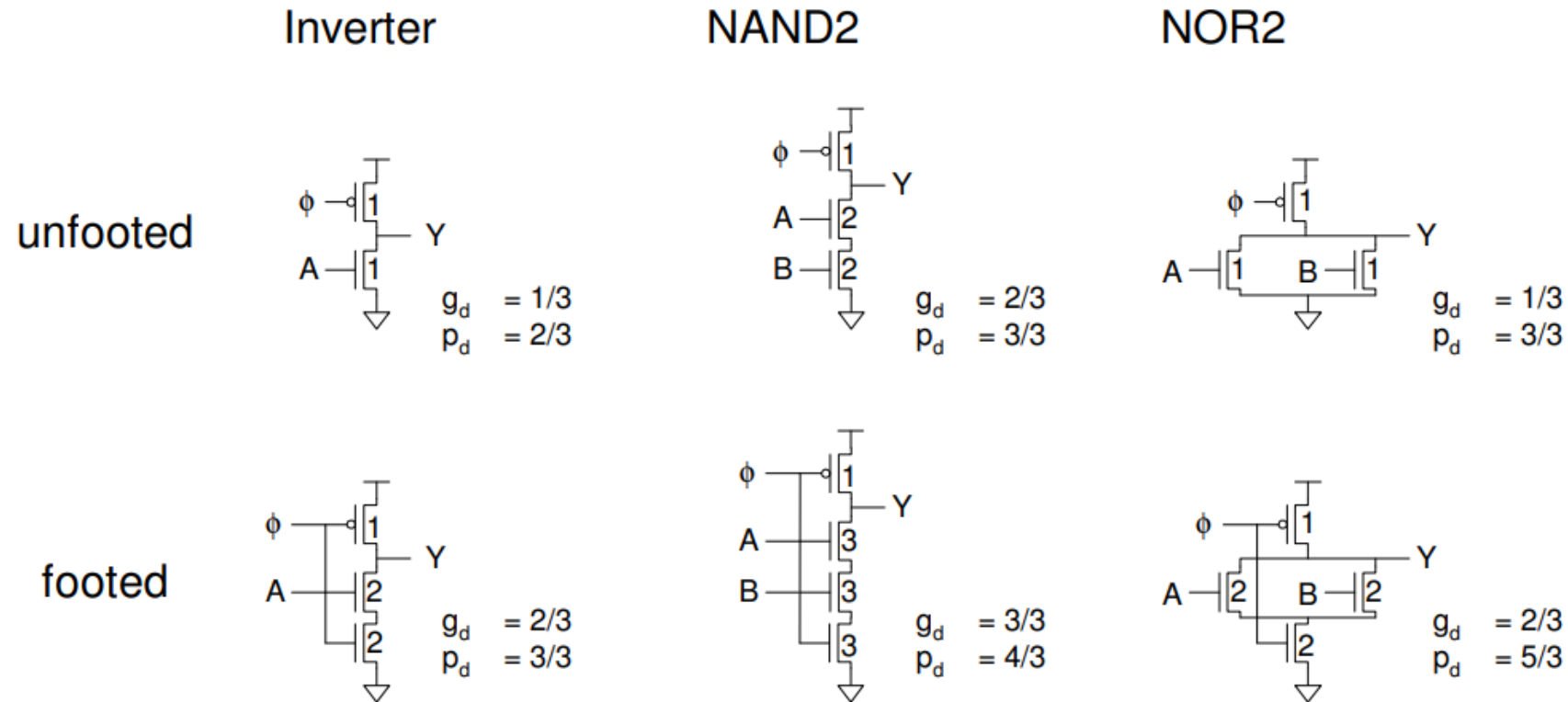

# Dynamic Logic Principles

## Dynamic Logic: Principles

 

### • Precharge

$\Phi = 0$ , *Out* is precharged to  $V_{DD}$  by  $M_p$ .  
 $M_e$  is turned off, no dc current flows  
 (regardless of input values)

### • Evaluation

$\Phi = 1$ ,  $M_e$  is turned on,  $M_p$  is turned off.  
 Output is pulled down to zero depending  
 on the values on the inputs. If not,  
 precharged value remains on  $C_L$ .


**Important:** Once *Out* is discharged, it cannot be charged again!  
 Gate input can make only one transition during evaluation

- Minimum clock frequency must be maintained
- Can  $M_e$  be eliminated?




# Dynamic Logic Example

## Example

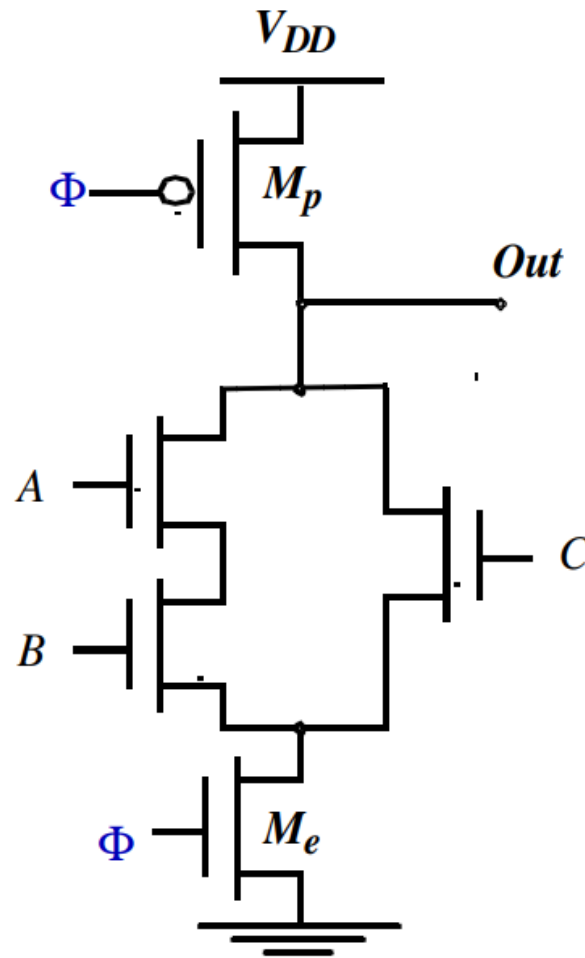

- **Ratioless**
- **No Static Power Consumption**
- **Noise Margins small ( $NM_L$ )**
- **Requires Clock**

# Evolution from Static Gate to Dynamic Gate

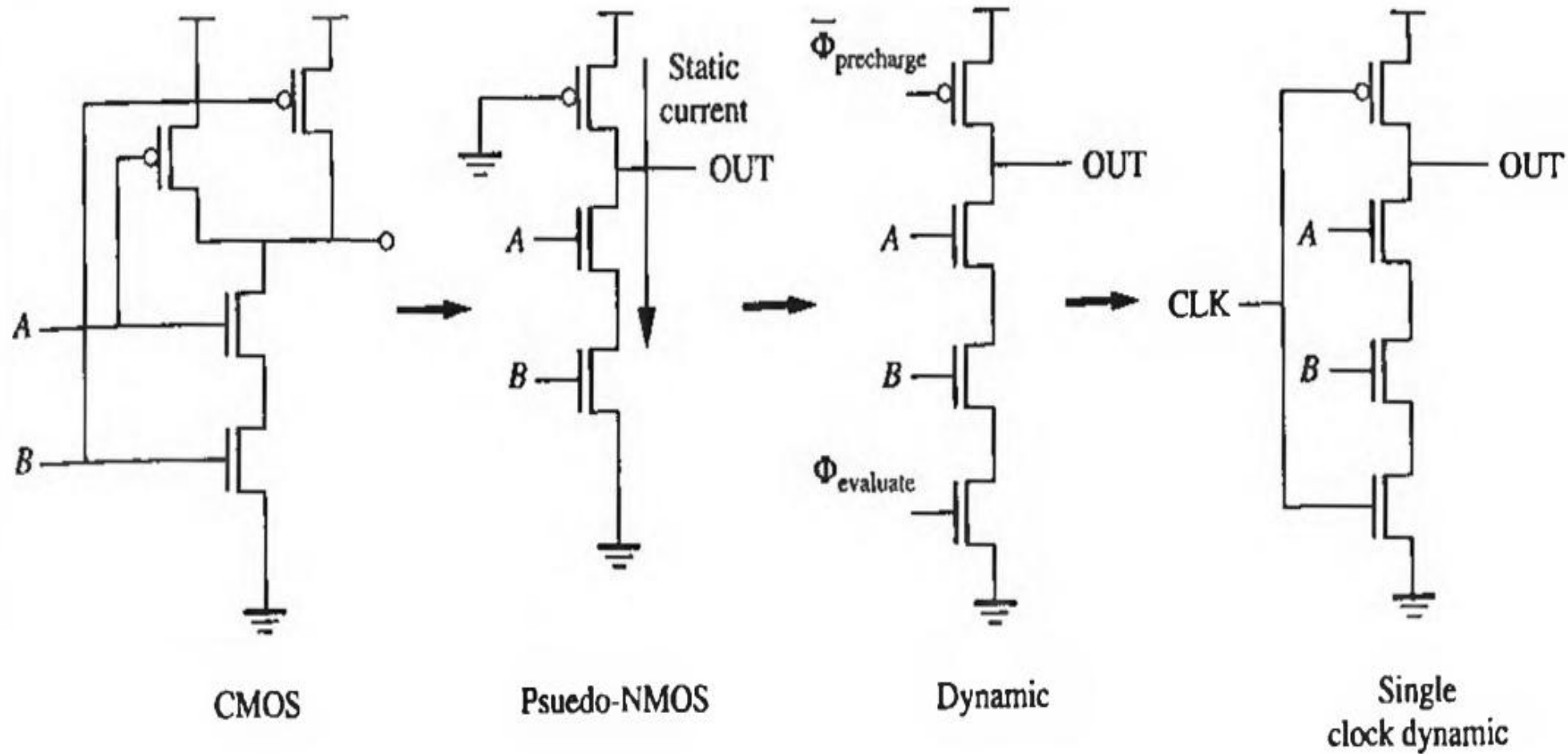


**Figure 7.25**

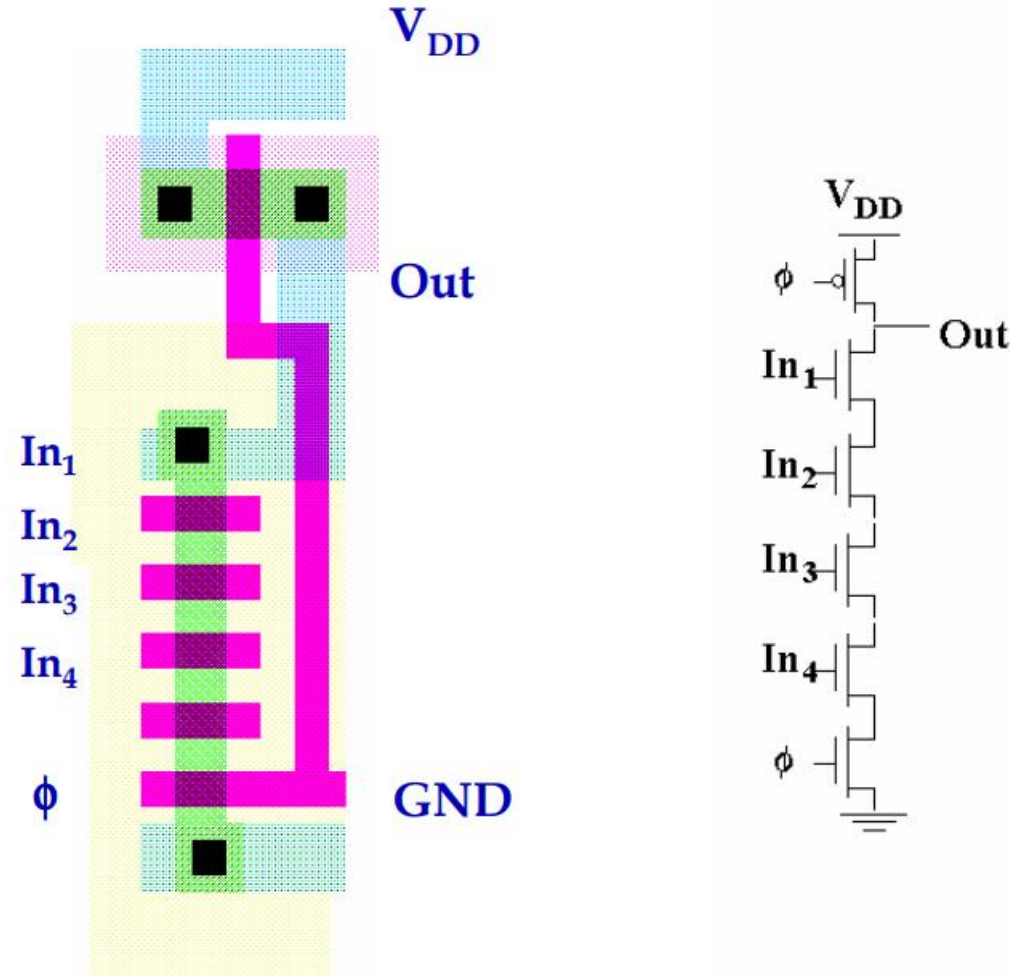Evolution from static gate to dynamic gate.

# Dynamic 4 Input NAND Gate

## Dynamic 4 Input NAND Gate



## Dynamic Gate Implementations


**Problem:**

Implement a 3-input NOR gate in dynamic logic and explain its operation. Size the transistors to deliver the same delays as a conventional CMOS inverter (PMOS  $8\lambda:2\lambda$ , NMOS  $4\lambda:2\lambda$ ).

 
**Solution:**

The dynamic 3-input NOR gate requires three parallel NMOS transistors, plus two transistors connected to the CLK input: one PMOS pull-up and one NMOS foot transistor. When CLK is low, the precharge transistor pulls the output to  $V_{DD}$ . When the clock goes high, the evaluate transistor turns on. If A or B or C is high, the output will be discharged to Gnd. If all three inputs are low, the output will remain high.

The pull-up requires a width of  $8\lambda$  to deliver the same rise delay as the CMOS inverter. This is somewhat irrelevant since all gates are precharged simultaneously. The pull-down tree should also be sized with  $8\lambda$  transistors to produce the equivalent  $4\lambda$  device to deliver the same fall delay as the CMOS inverter. The final sizes are shown below:



# LE of Static and Dynamic Gates

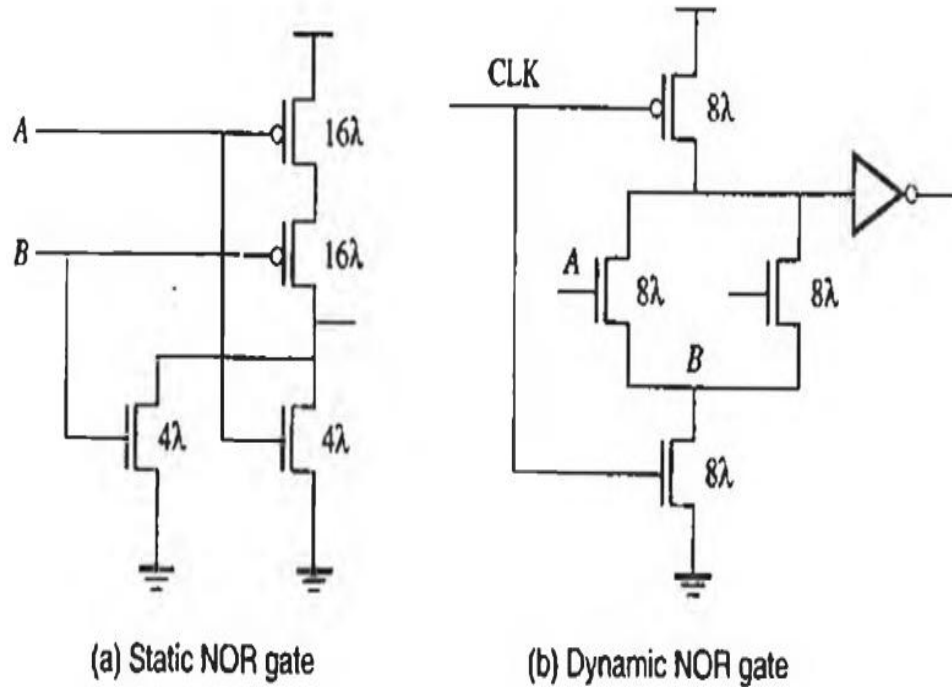

**Figure 7.29**  
Comparison of static and dynamic logical effort.

For the static gate, we already determined its logical effort to be  $5/3$ . This can be derived by comparing the input capacitance of the static NOR to a corresponding inverter. The inverter size of  $8\lambda$  for the pull-up and  $4\lambda$  for the pull-down produces a ratio of

$$LE_{\text{NOR}} = \frac{(\text{NOR input cap.})}{(\text{Inverter input cap.})} = \frac{16\lambda + 4\lambda}{8\lambda + 4\lambda} = 5/3$$


For the domino circuit, the input capacitance is simply  $8\lambda$  since it is only connected to NMOS devices. Then,

$$LE_{\text{dyn\_NOR}} = \frac{(\text{Dynamic input cap.})}{(\text{Inverter input cap.})} = \frac{8\lambda}{12\lambda} = 2/3$$

Since the extra inverter in domino logic has an  $LE = 1$ , the average LE for each of the two gates is the geometric mean of the product of their logical efforts (i.e.,  $LE_{\text{avg}} = \sqrt{(2/3)(1)} \approx 0.8$ ). Therefore, the domino stage is better in terms of its overall drive capability and input capacitive loading.

# Cascaded Dynamic Gates

## Cascading Dynamic Gates

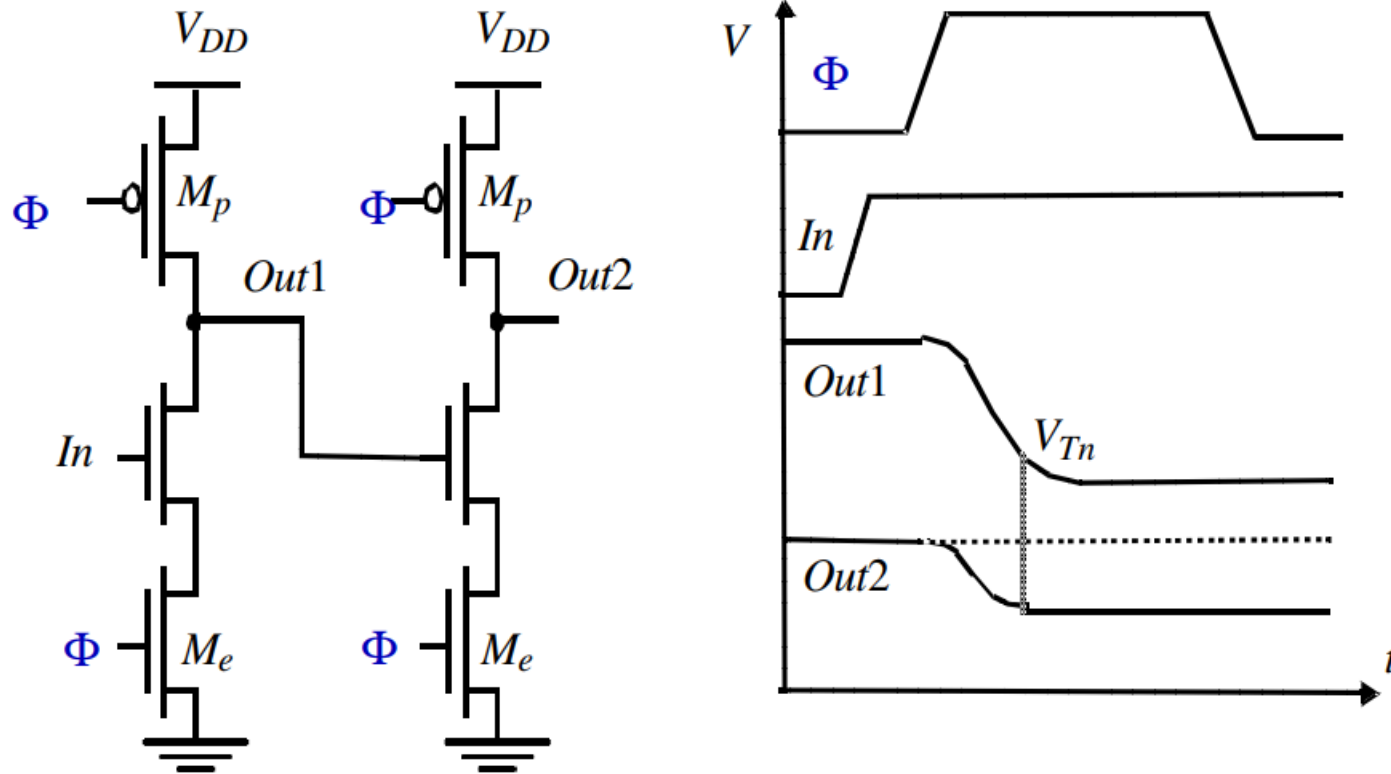


Internal nodes can only make 0-1 transitions during evaluation period

# Monotonicity in Dynamic Gates
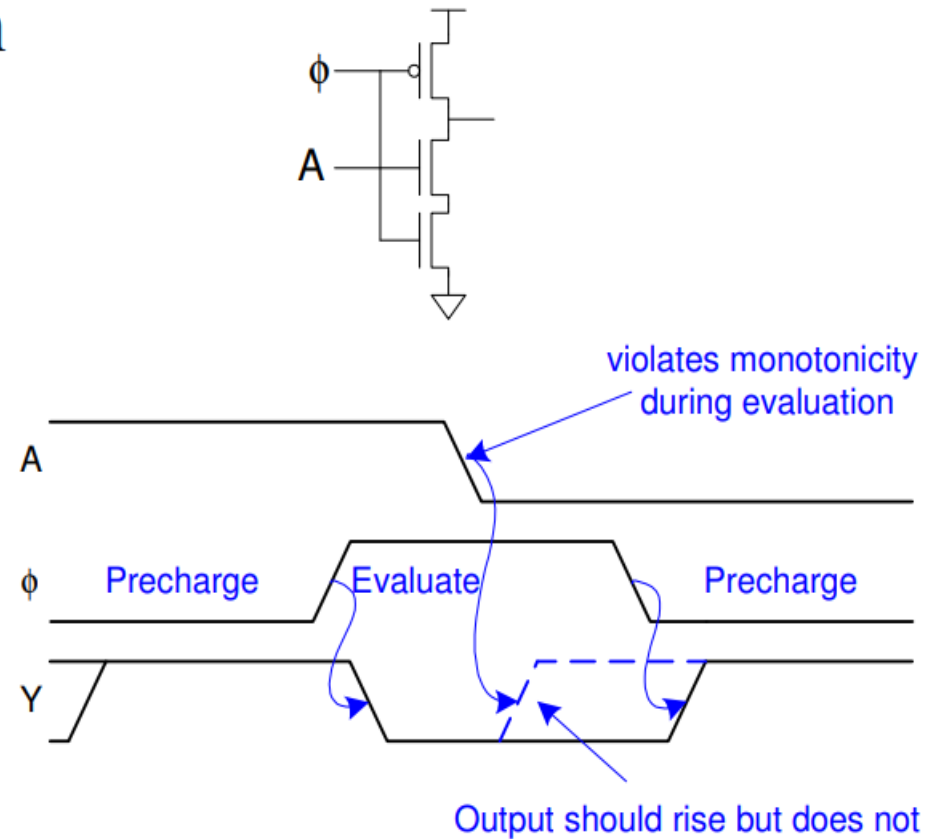
## Monotonicity

- Dynamic gates require *monotonically rising* inputs during evaluation
  - 0  $\rightarrow$  0
  - 0  $\rightarrow$  1
  - 1  $\rightarrow$  1
  - But not 1  $\rightarrow$  0







# Monotonicity Problems in Dynamic Gates
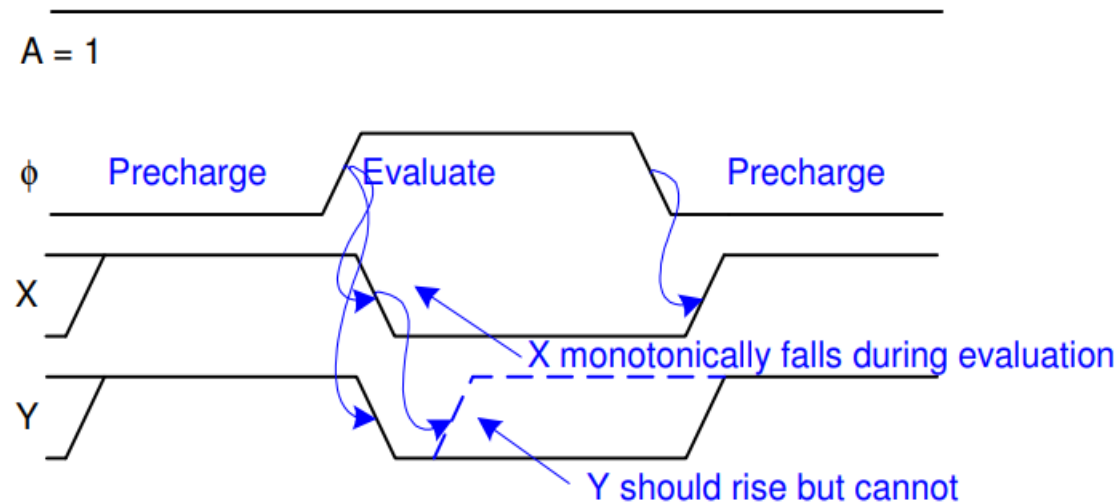 
## Monotonicity Woes


- But dynamic gates produce monotonically falling outputs during evaluation
- Illegal for one dynamic gate to drive another!






# Reliability Issues in Dynamic Gates

## Reliability Problems — Charge Leakage

 

(a) Leakage sources

 

(b) Effect on waveforms

$A = 0$

(1) Leakage through reverse-biased diode of the diffusion area


(2) Subthreshold current from drain to source

**Minimum Clock Frequency: > 1 MHz**

# Charge Leakage in Dynamic Gates
 
## Leakage



- Dynamic node floats high during evaluation
  - Transistors are leaky ( $I_{OFF} \neq 0$ )
  - Dynamic value will leak away over time
  - Formerly milliseconds, now nanoseconds!
- Use keeper to hold dynamic node
  - Must be weak enough not to fight evaluation



# What is Charge Sharing?
  
## Charge Sharing

- Dynamic gates suffer from charge sharing




$$V_x = V_Y = \frac{C_Y}{C_x + C_Y} V_{DD}$$



# Charge Sharing in Dynamic Gates
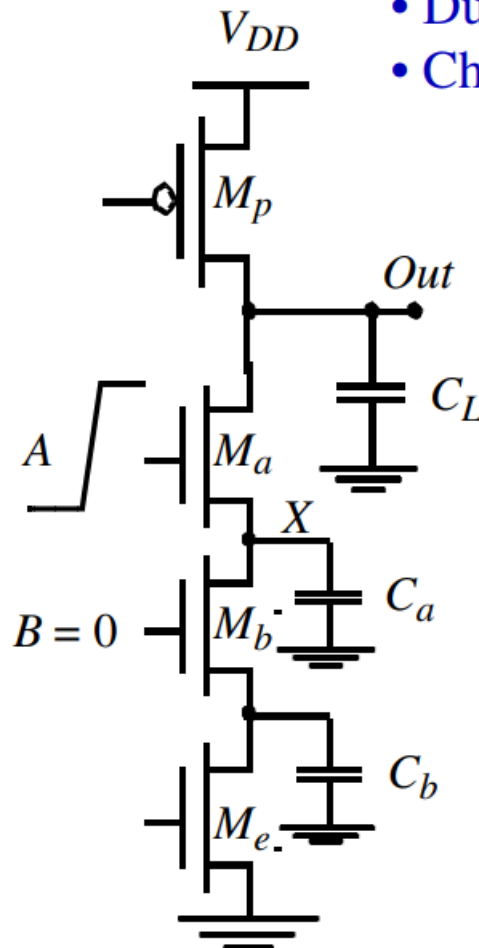
## Charge Sharing (redistribution)

- Assume: during precharge, A and B are 0,  $C_a$  is discharged
- During evaluation, B remains 0 and A rises to 1
- Charge stored on  $C_L$  is now redistributed over  $C_L$  and  $C_a$



$$C_L V_{DD} = C_L V_{out}(t) + C_a V_X$$


$$V_X = V_{DD} - V_t, \text{ therefore}$$

$$\delta V_{out}(t) = V_{out}(t) - V_{DD} = -\frac{C_a}{C_L} (V_{DD} - V_t)$$


Desirable to keep the voltage drop below threshold of pMOS transistor (why?)  $\Rightarrow C_a/C_L < 0.2$

# Charge Redistribution

## Charge Redistribution - Solutions

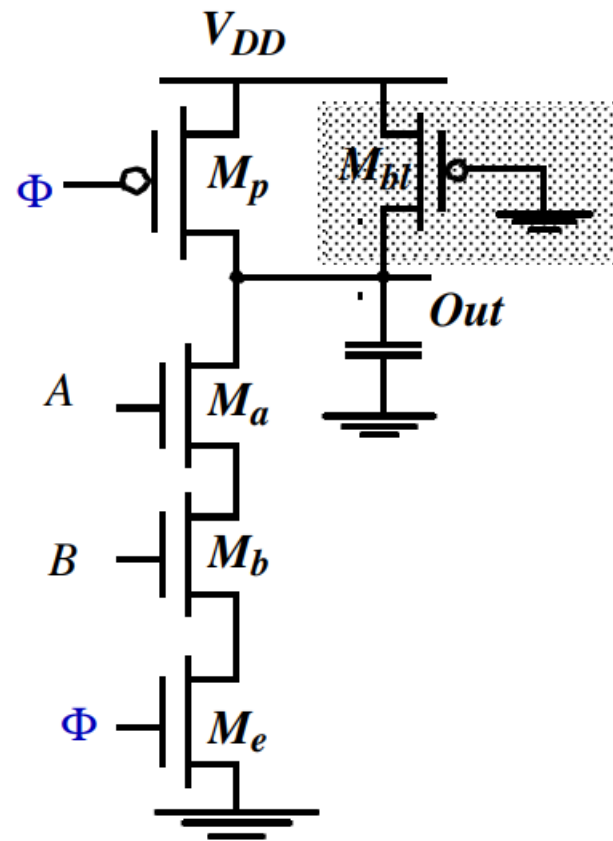

(a) Static bleeder

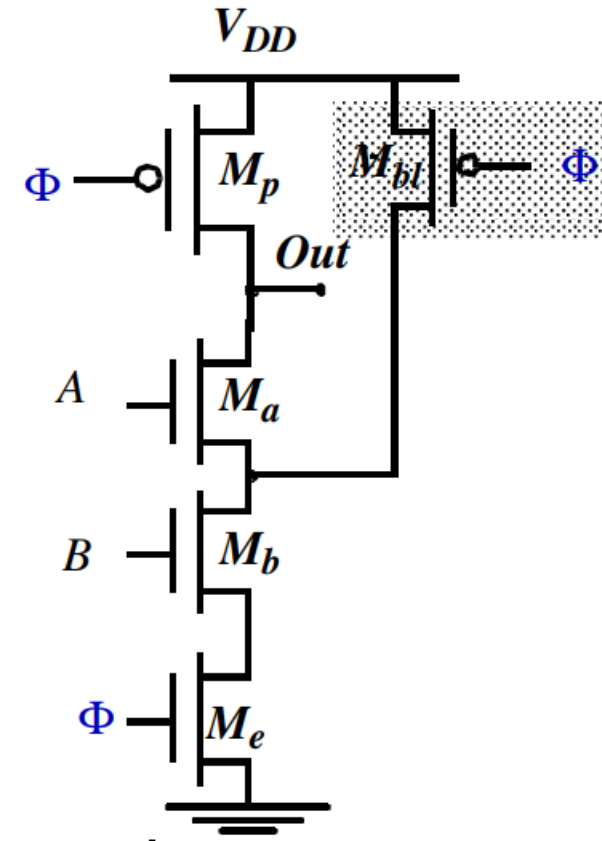


(b) Precharge of internal nodes

# Secondary Precharge in Dynamic Gates
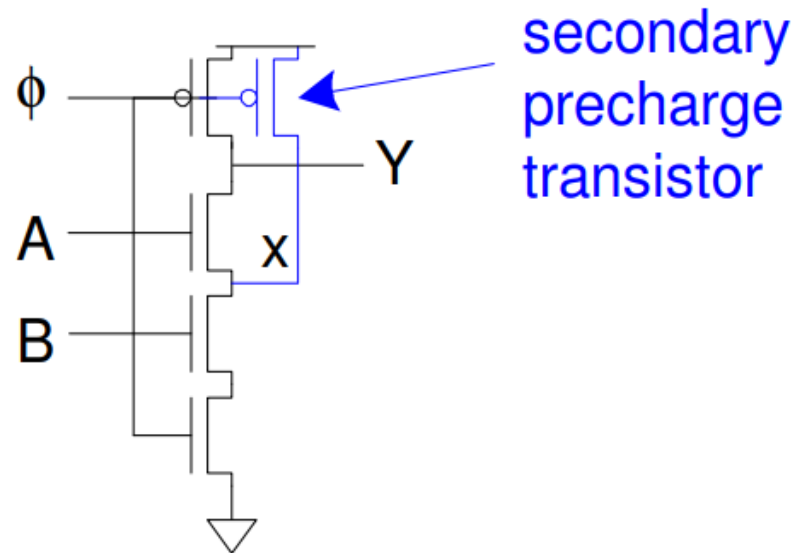
## Secondary Precharge

- Solution: add secondary precharge transistors
  - Typically need to precharge every other node
- Big load capacitance  $C_Y$  helps as well




# Domino Logic




# What is Domino Logic?

## Domino Logic

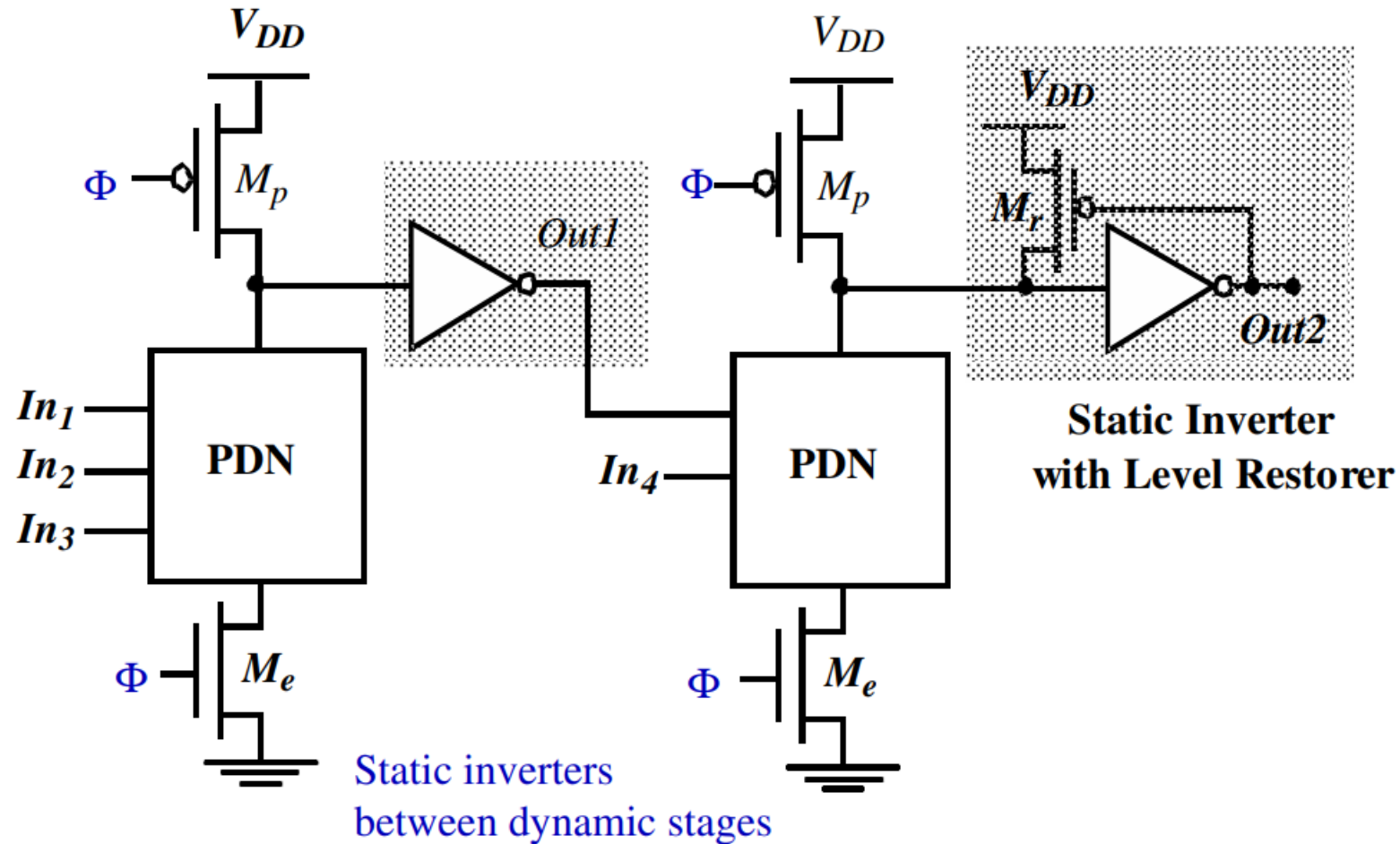

# Charge Retention Using Keeper Transistors

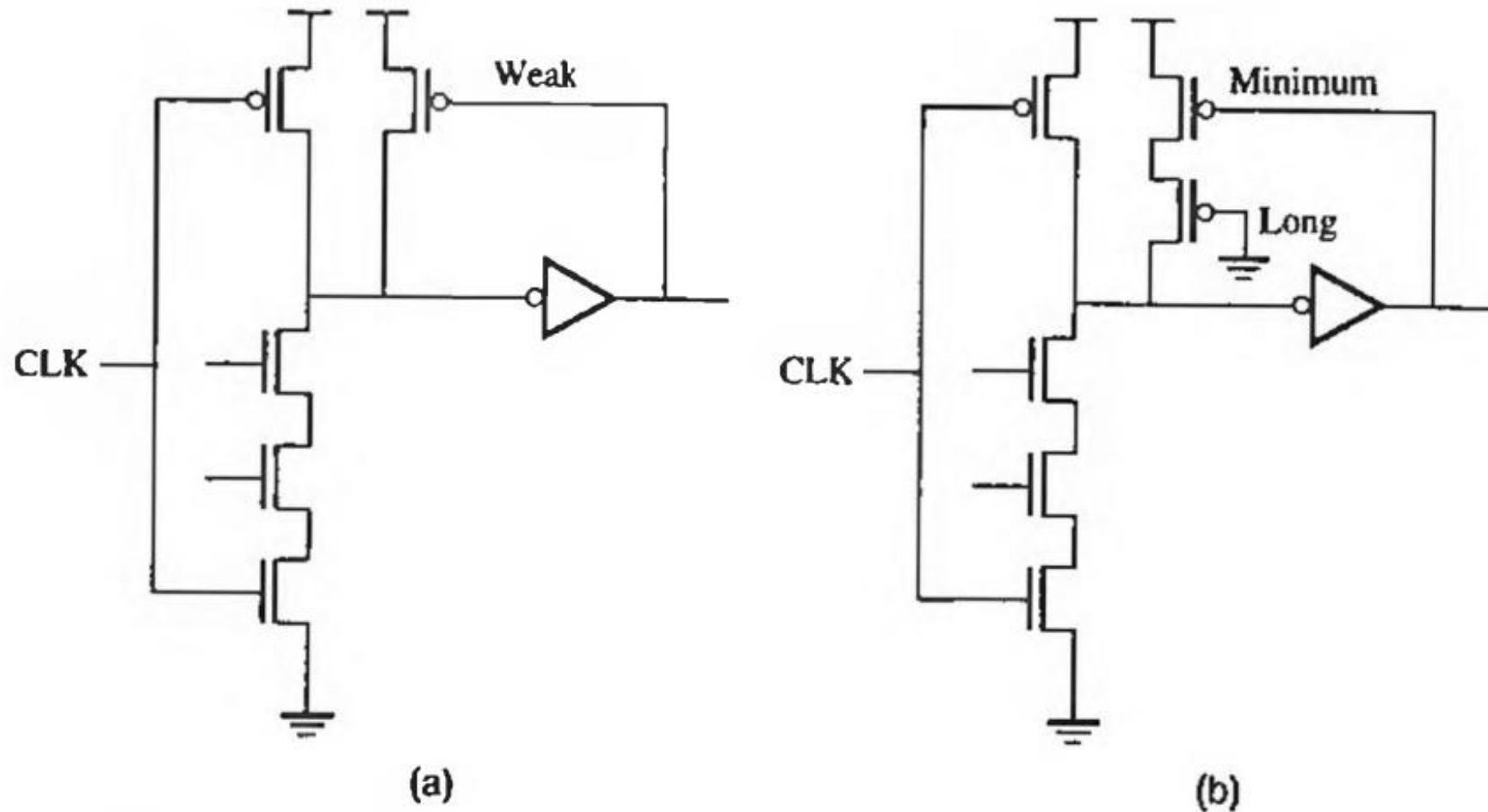


**Figure 7.31**

 Minimizing the effects of charge sharing using keepers.

# Domino Cascaded Gates

A cascade of three domino logic stages is shown in Figure 7.28. All three stages are precharged high when  $\Phi$  is low. The clock,  $\Phi$ , need not be low for very long since all stages are precharged simultaneously. In fact, the clock should only be low until all inverter outputs are low. When  $\Phi$  goes high, we enter the evaluation phase where the internal nodes (labeled  $Y_1, Y_2, Y_3$ ) will fall like dominos in order from left to right, assuming there is a path to the Gnd through their respective  $n$ -complexes. This is why the name *domino* is used to describe logic circuits implemented in this fashion.


 
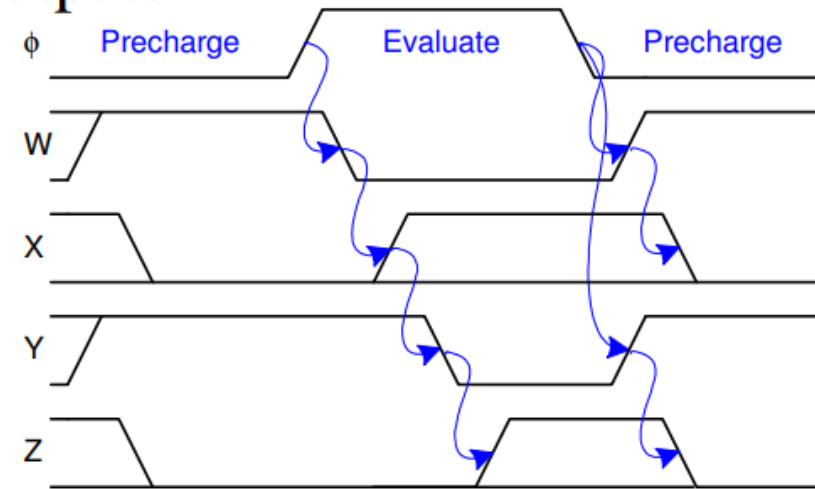


**Figure 7.28**  
Domino cascaded gates.

# Domino Gate Operation
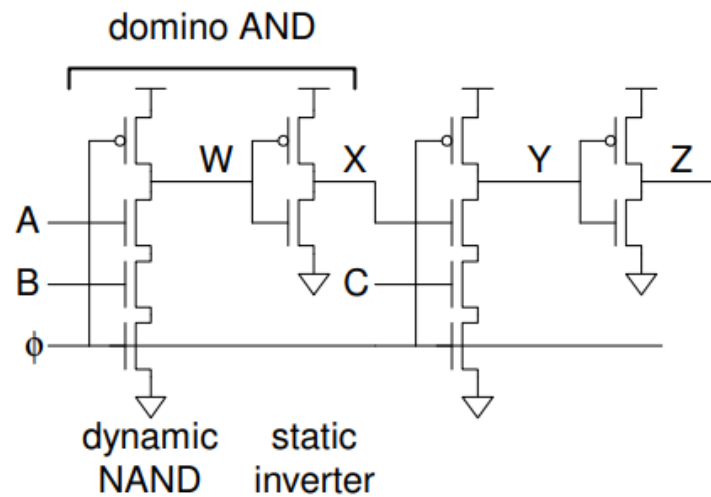
## Domino Gates

- Follow dynamic stage with inverting static gate
  - Dynamic / static pair is called domino gate
  - Produces monotonic outputs




## Domino Logic - Characteristics

- Only non-inverting logic
- Very fast - Only 1->0 transitions at input of inverter
- Precharging makes pull-up very fast
- Adding level restorer reduces leakage and charge redistribution problems
- Optimize inverter for fan-out

# Domino Gates Optimization
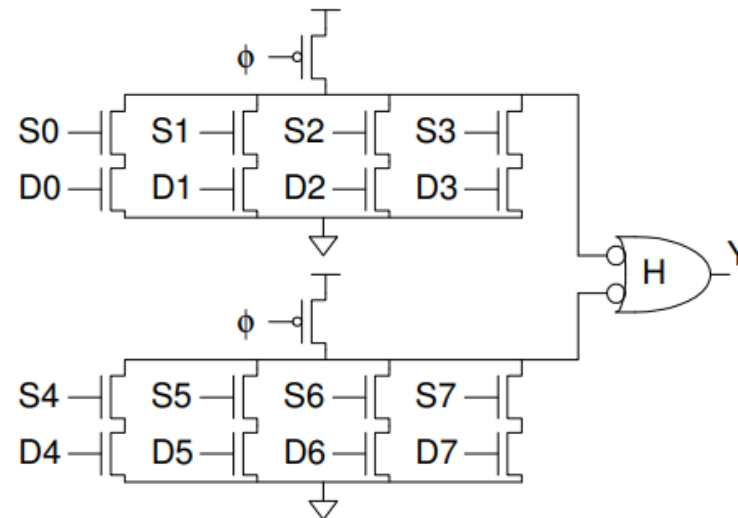
## Domino Optimizations


- Each domino gate triggers next one, like a string of dominos toppling over
- Gates evaluate sequentially but precharge in parallel
- Thus evaluation is more critical than precharge
- HI-skewed static stages can perform logic



## Dual-Rail Domino

- Domino only performs noninverting functions:
  - AND, OR but not NAND, NOR, or XOR
- Dual-rail domino solves this problem
  - Takes true and complementary inputs
  - Produces true and complementary outputs


sig_h	sig_l	Meaning
0	0	Precharged
0	1	'0'
1	0	'1'
1	1	invalid

 

# Dual Rail AND/NAND
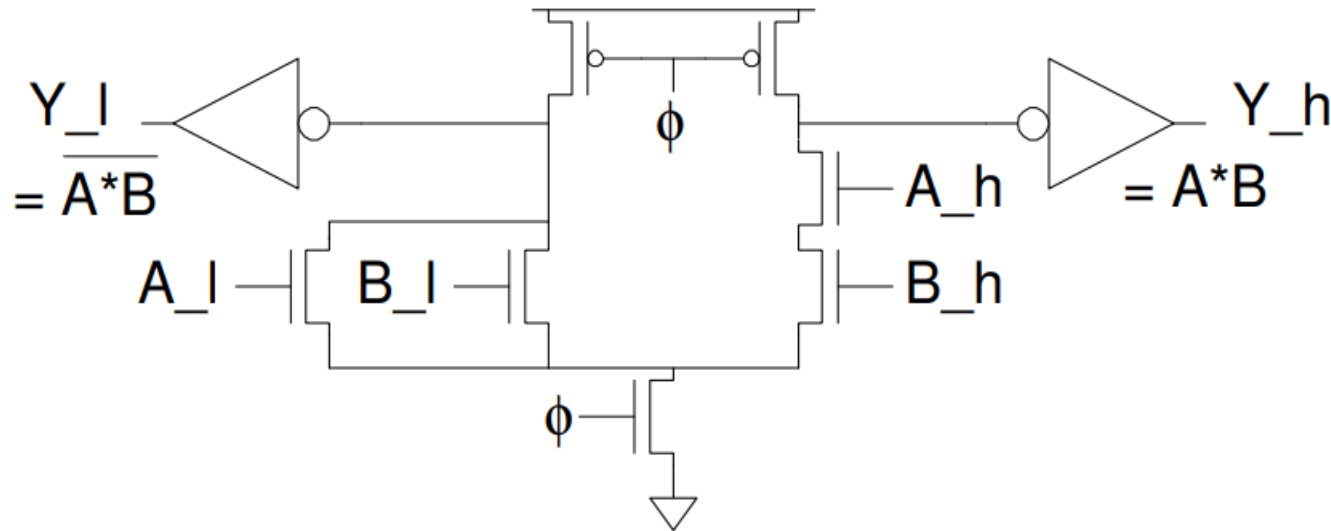
## Example: AND/NAND


- Given  $A_h, A_l, B_h, B_l$
- Compute  $Y_h = A * B, Y_l = \sim(A * B)$
- Pulldown networks are conduction complements




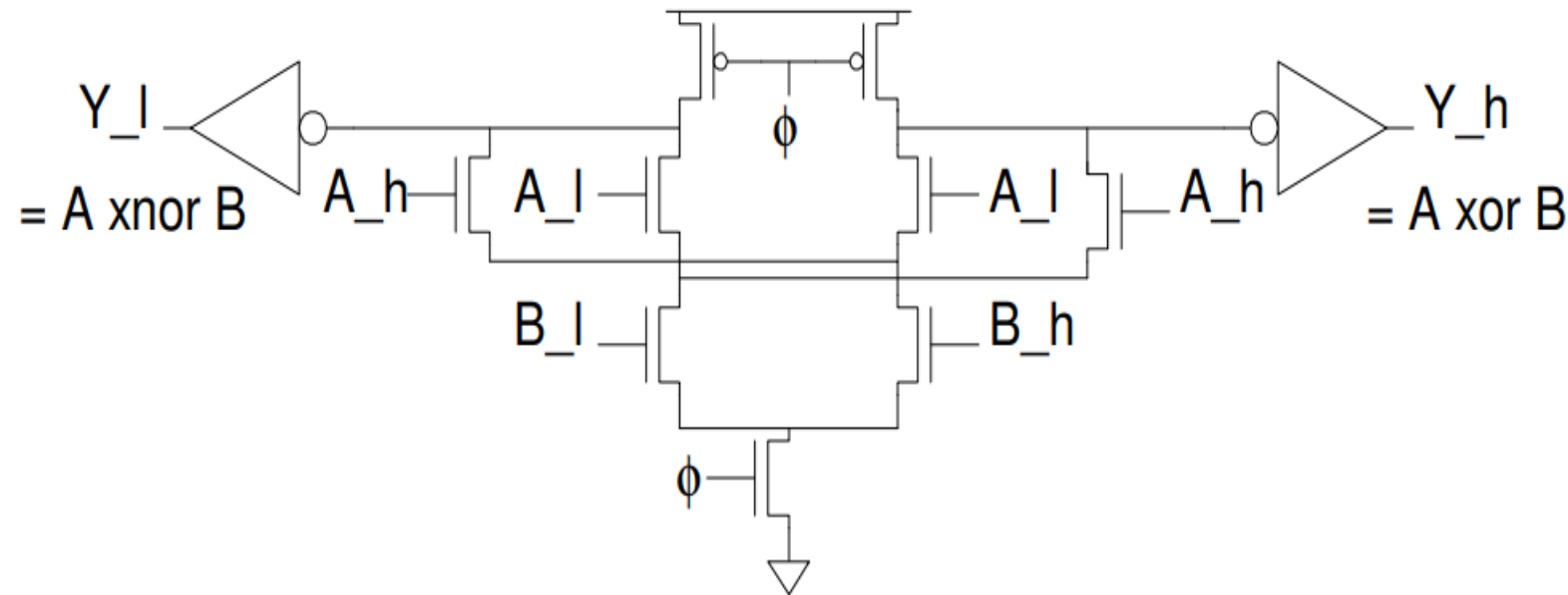
## Example: XOR/XNOR


- Sometimes possible to share transistors



## Domino Summary

- Domino logic is attractive for high-speed circuits
  - 1.5 – 2x faster than static CMOS
  - But many challenges:
    - Monotonicity
    - Leakage
    - Charge sharing
    - Noise
- Widely used in high-performance microprocessors


## np-CMOS (Zipper CMOS)

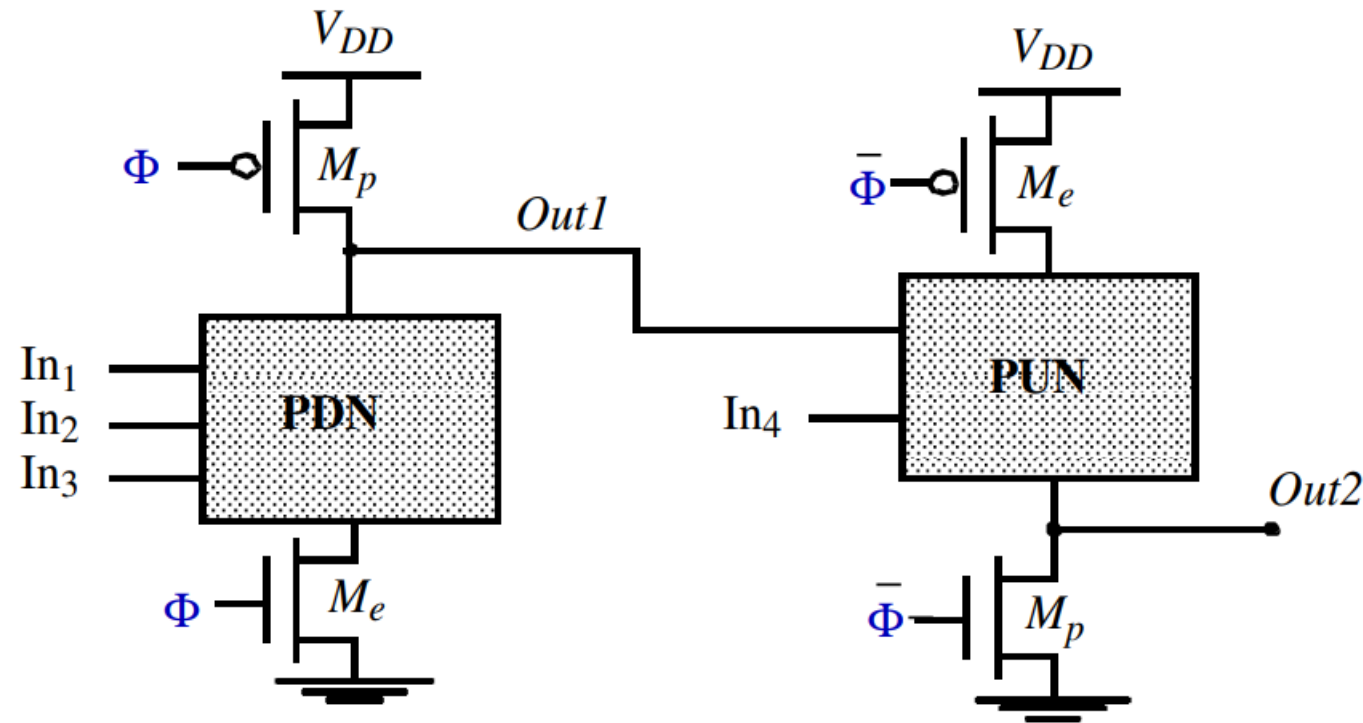

- Only 1-0 transitions allowed at inputs of PUN
- Used a lot in the Alpha design

# NP Zipper CMOS Adder

## np CMOS Adder

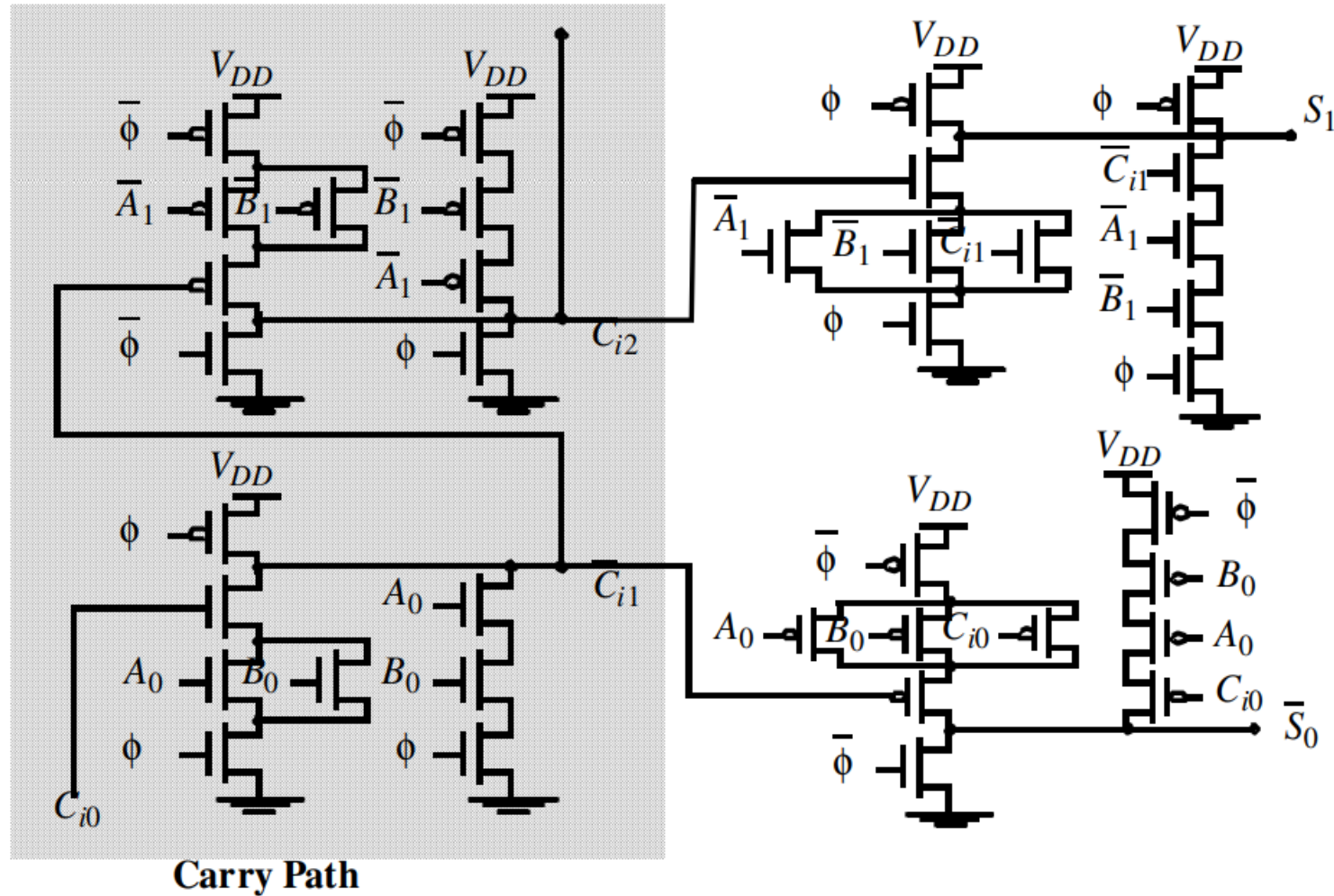

- Combinational Circuit Families are discussed in Chapter 9 of course textbook CMOS VLSI Design by Weste and Harris, 4<sup>th</sup> Ed.