

CS250

VLSI Systems Design

Fall 2020



John Wawrzynek

with

Arya Reais-Parsi

MOSFET Threshold Voltage

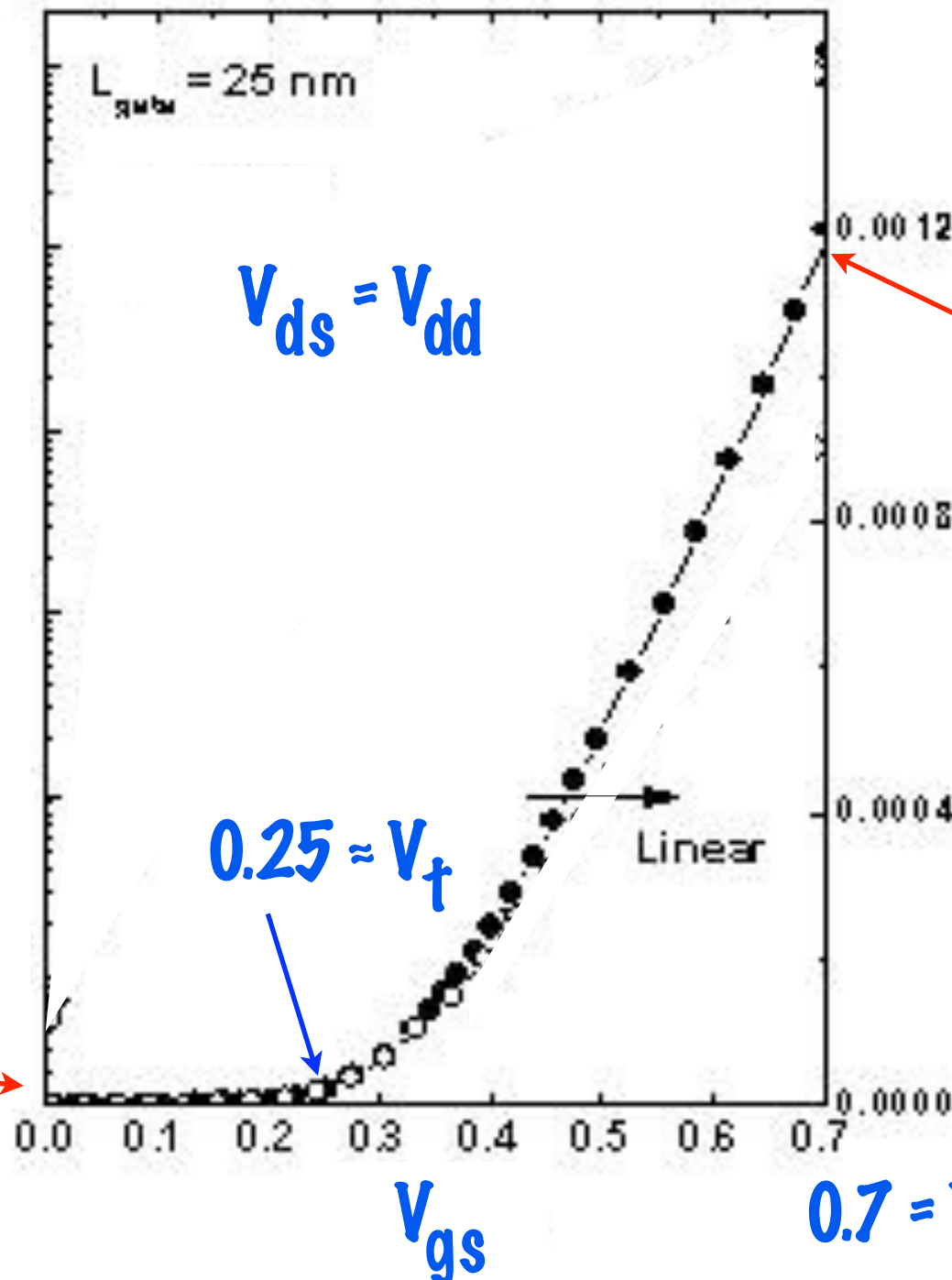 Transistor “turns on” when V_{gs} is $> V_t$.



$I_{off} = 0$

$V_{ds} = V_{dd}$

$1.2 \text{ mA} = I_{on}$

I_{ds}





$0.25 \approx V_t$

Linear

V_{gs}

$0.7 = V_{dd}$


CMOS Transistor Limitations

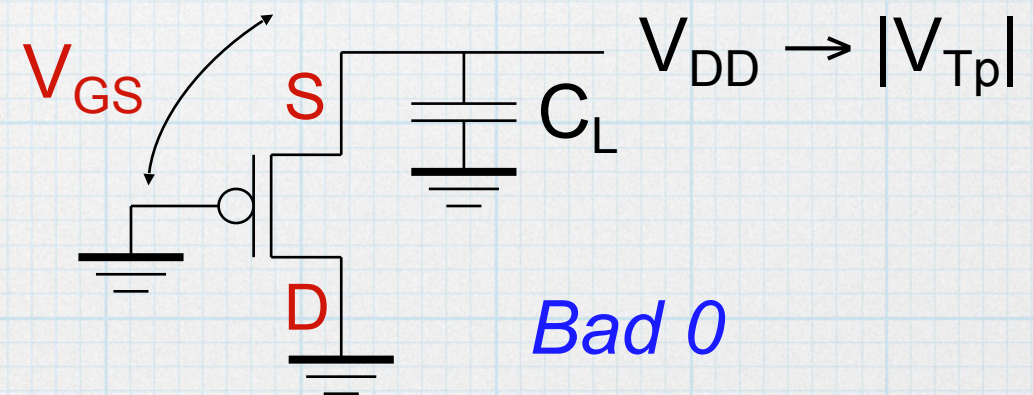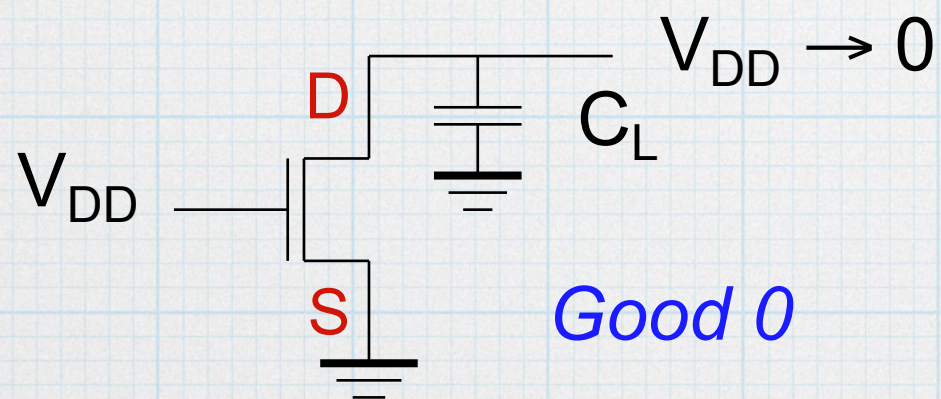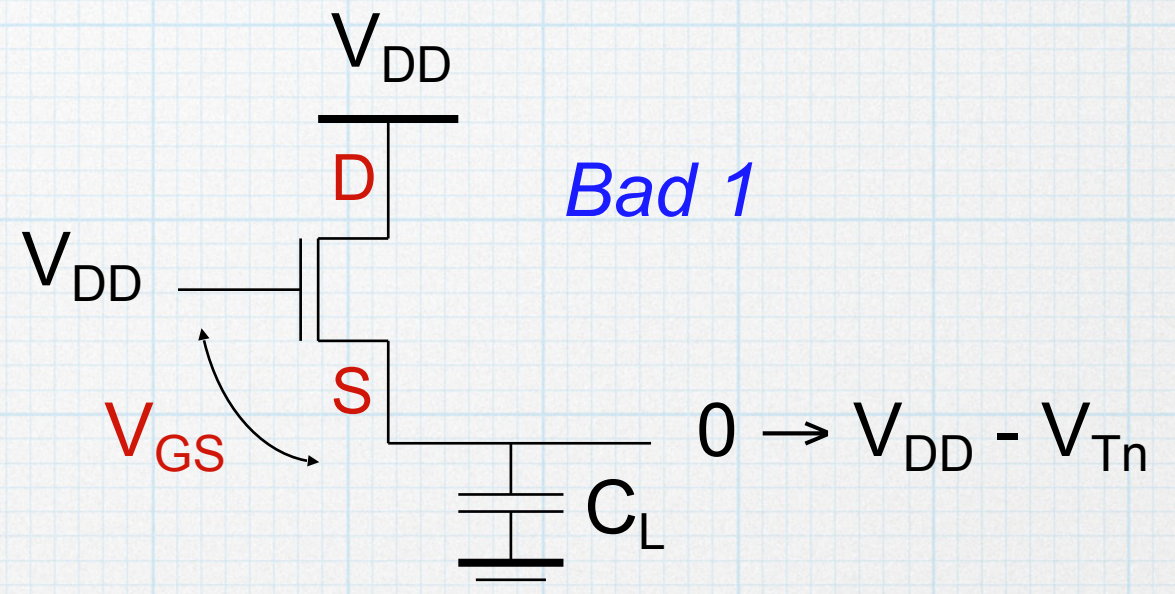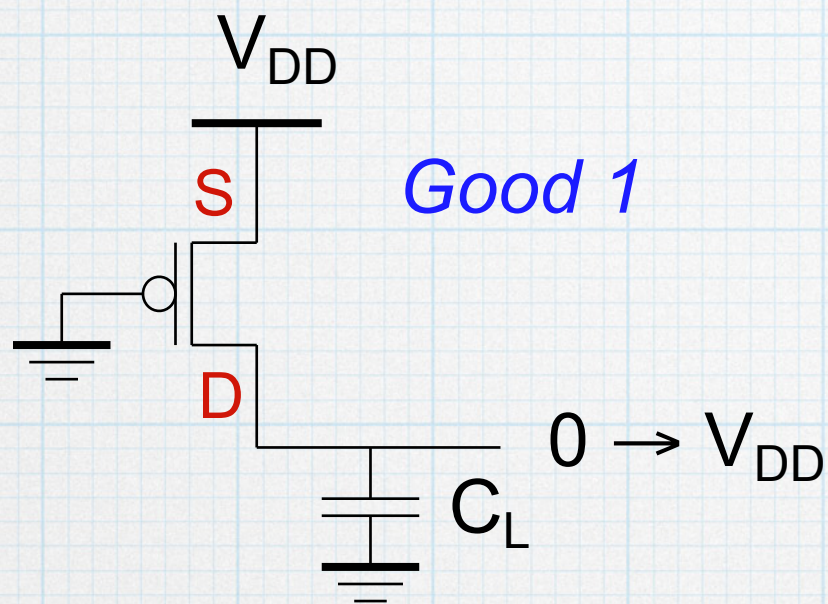

Tough luck ...

Transmission Gate

 - ▶ Transmission gates are the way to build ideal “switches” in CMOS.
- ▶ In general, both transistor types are needed:
 - ❑ nFET to pass zeros.
 - ❑ pFET to pass ones.




if $en == 1$ then A connects to B



Transmission-gate Multiplexor

2-to-1 multiplexor:

$$c = sa + s'b$$

 


Switches simplify the implementation:

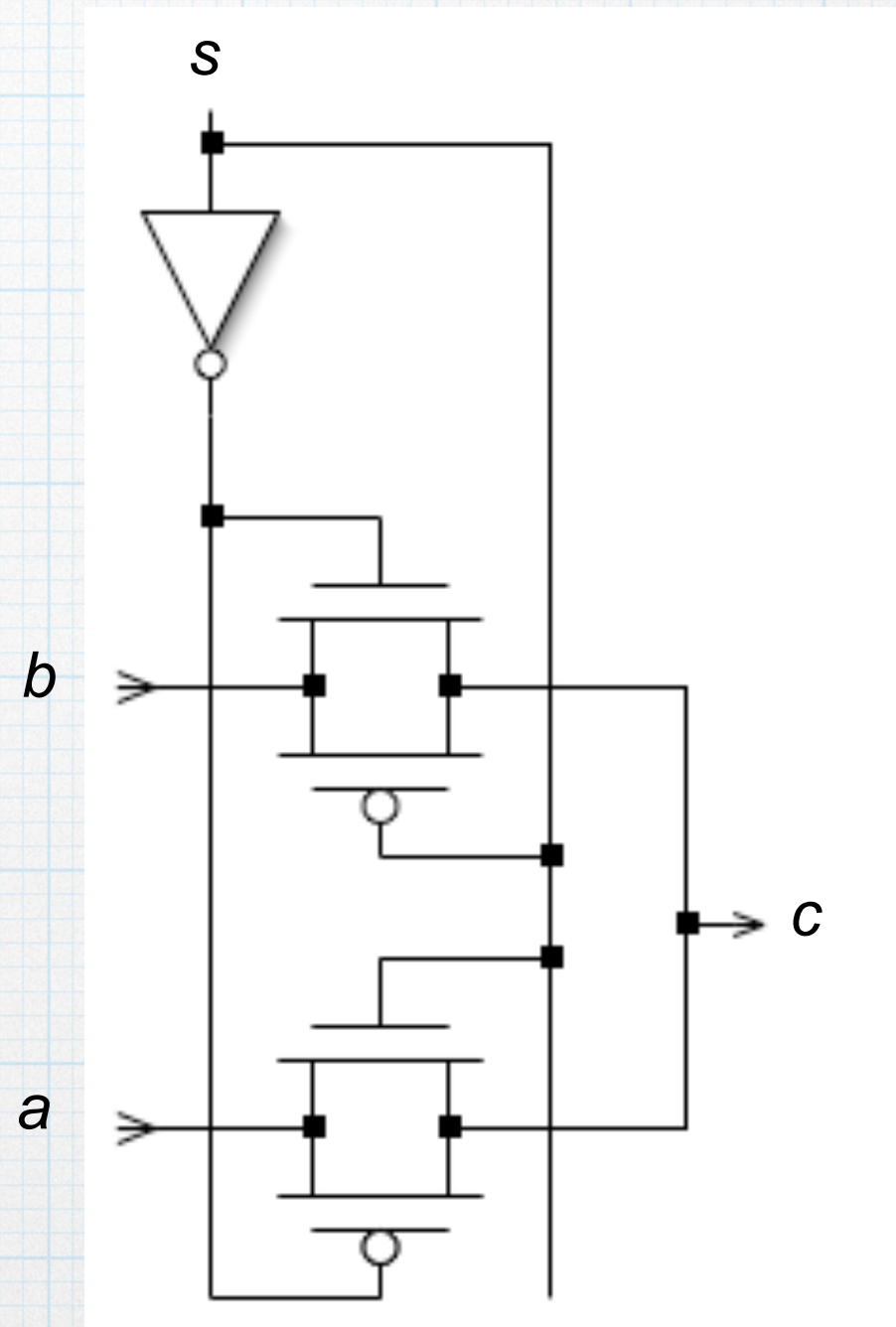 

Compare the cost to logic gate implementation.


Larger Multiplexors

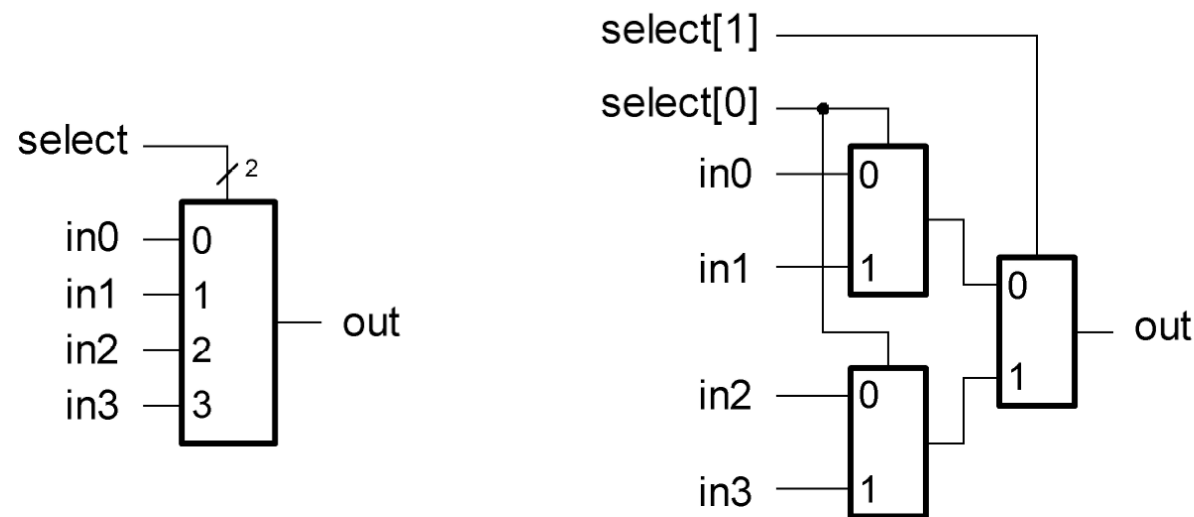

a) 4-input mux symbol


b) 4-input mux implemented with 2-input muxes

Care must be taken to not string together many pass-transistor stages. Occasionally, need to “rebuffer” with static gate (or inverter).

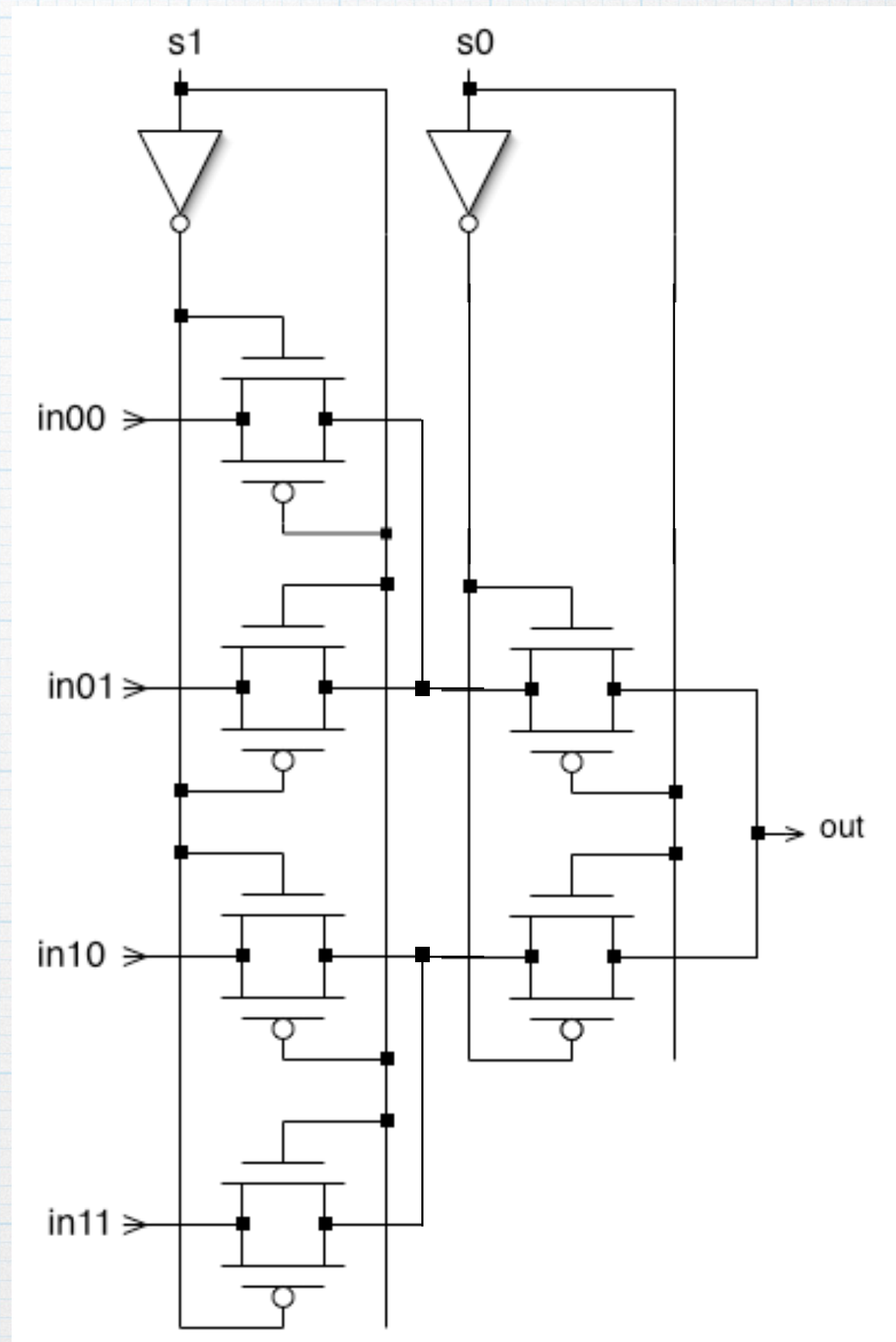


Predecoded 4-to-1 Multiplexor

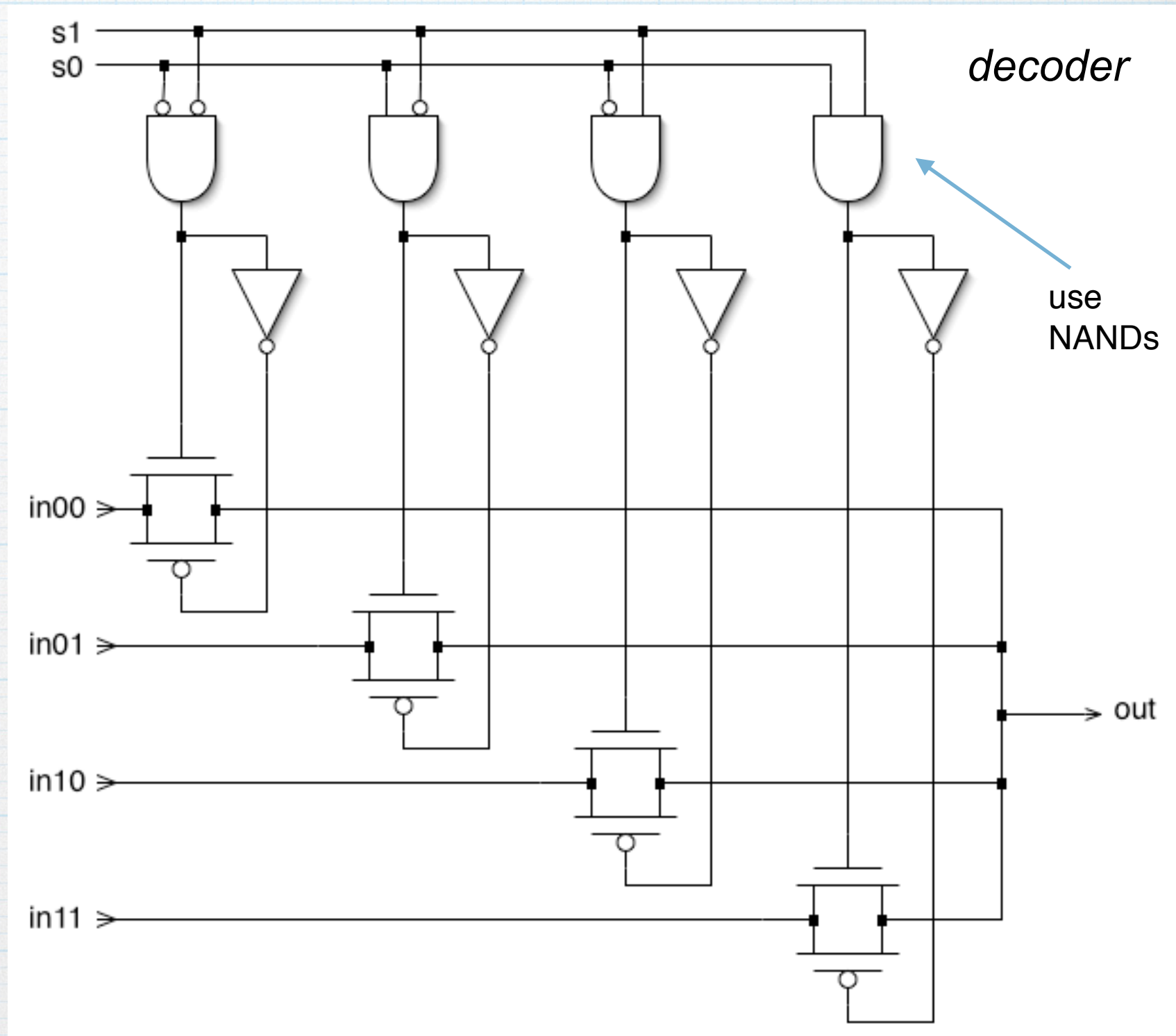- ▶ This version has less delay from in to out.
- ▶ In both versions, care must be taken to avoid turning on multiple paths simultaneously (shorting together the inputs).



Tri-state Buffers


Tri-state Buffer:

 

OE	IN	OUT
0	0	Z
0	1	Z
1	0	0
1	1	1


“high impedance” (output disconnected)

Variations:

 

OE	IN	OUT
0	-	Z
1	0	1
1	1	0



Inverting buffer

 

OE	IN	OUT
0	0	0
0	1	1
1	-	Z

Inverted enable


CMOS Implementation

  



*transmission gate provide the isolation:
usually designed this way*

Tri-state Based Multiplexor



Multiplexor:

 




If $s=1$ then $c=a$ else $c=b$

  

 
 
Transistor Circuit for inverting-multiplexor:





Sky130 Stdcell Multiplexor

   

LUT implementation

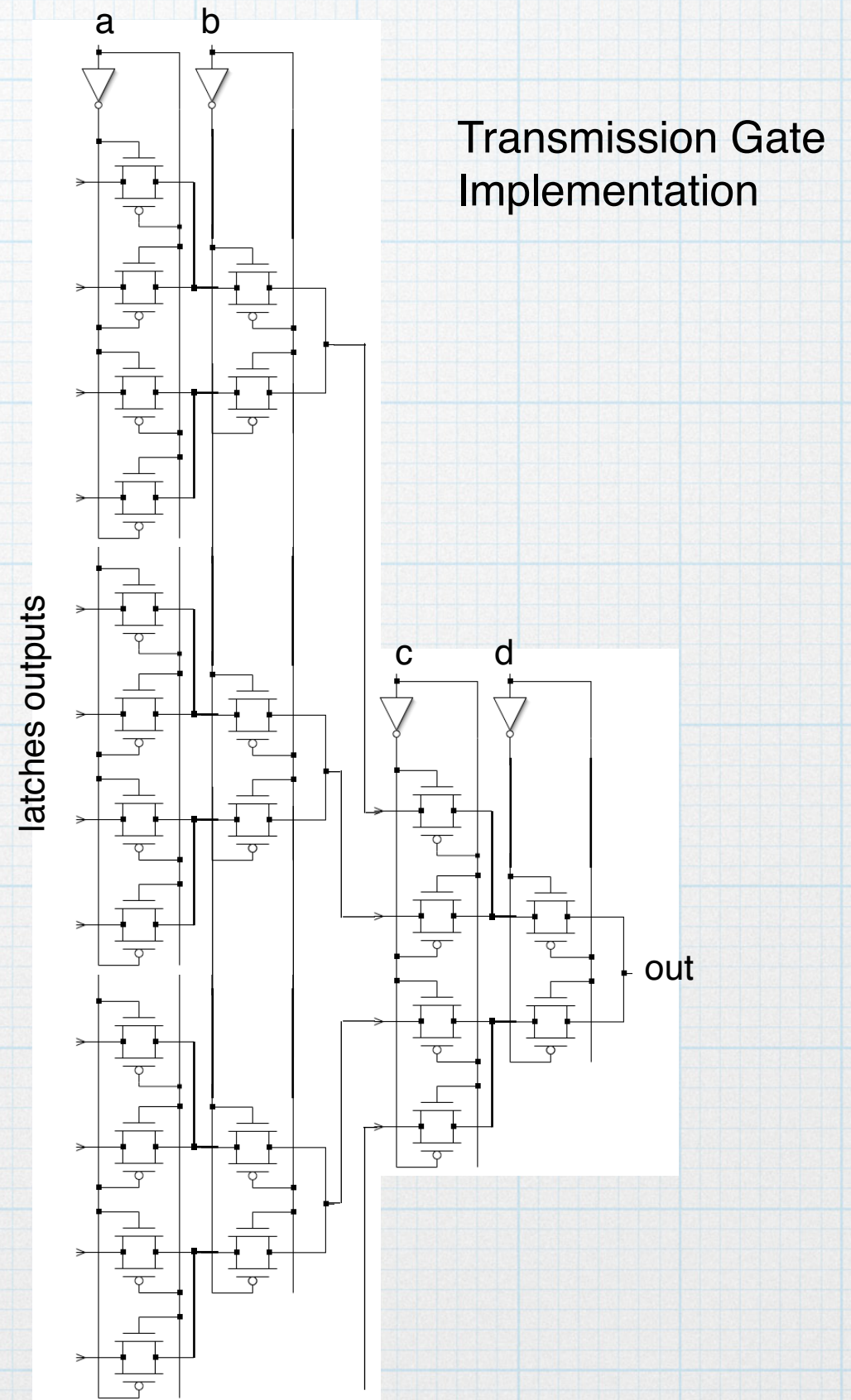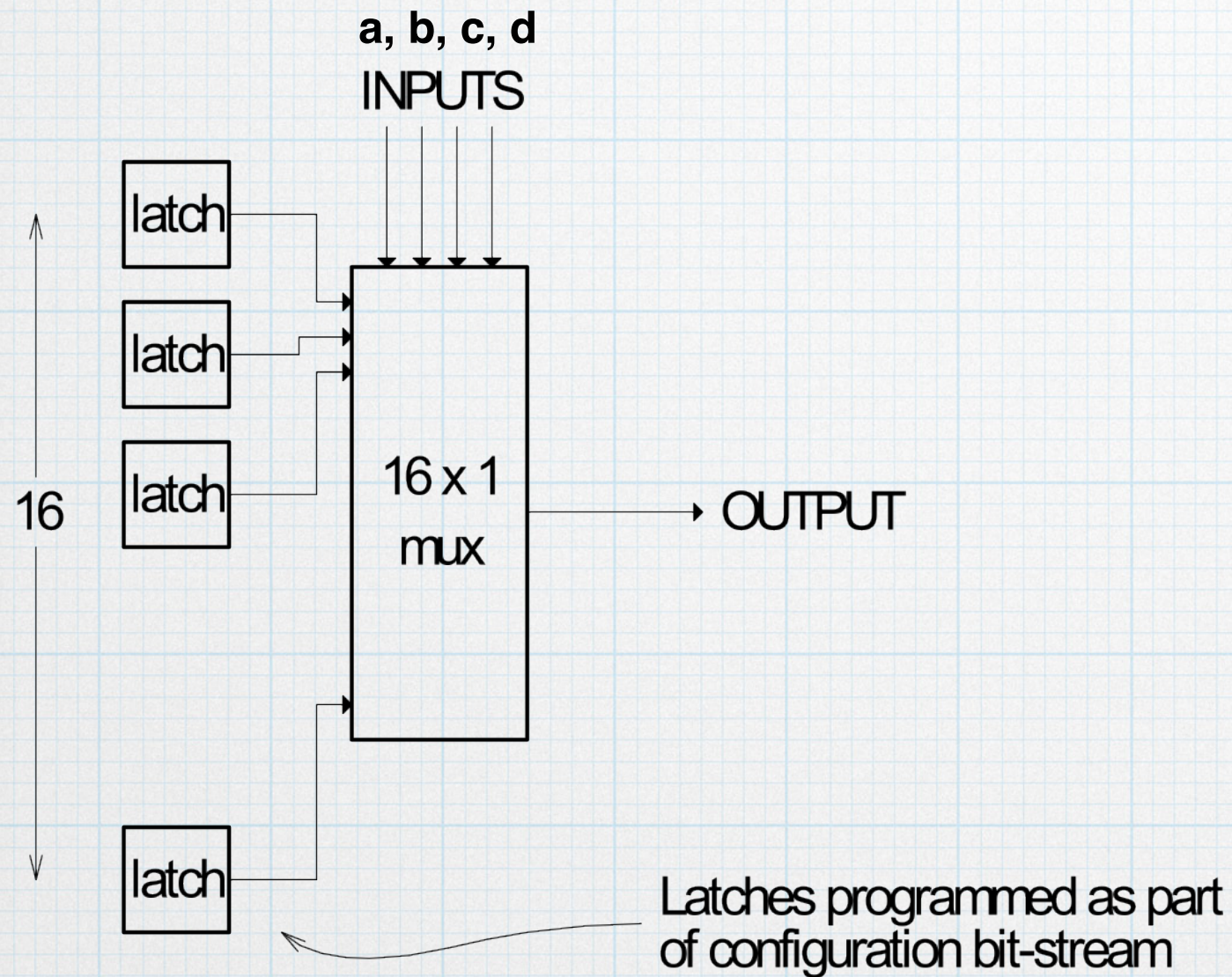



Higher Performance LUTs

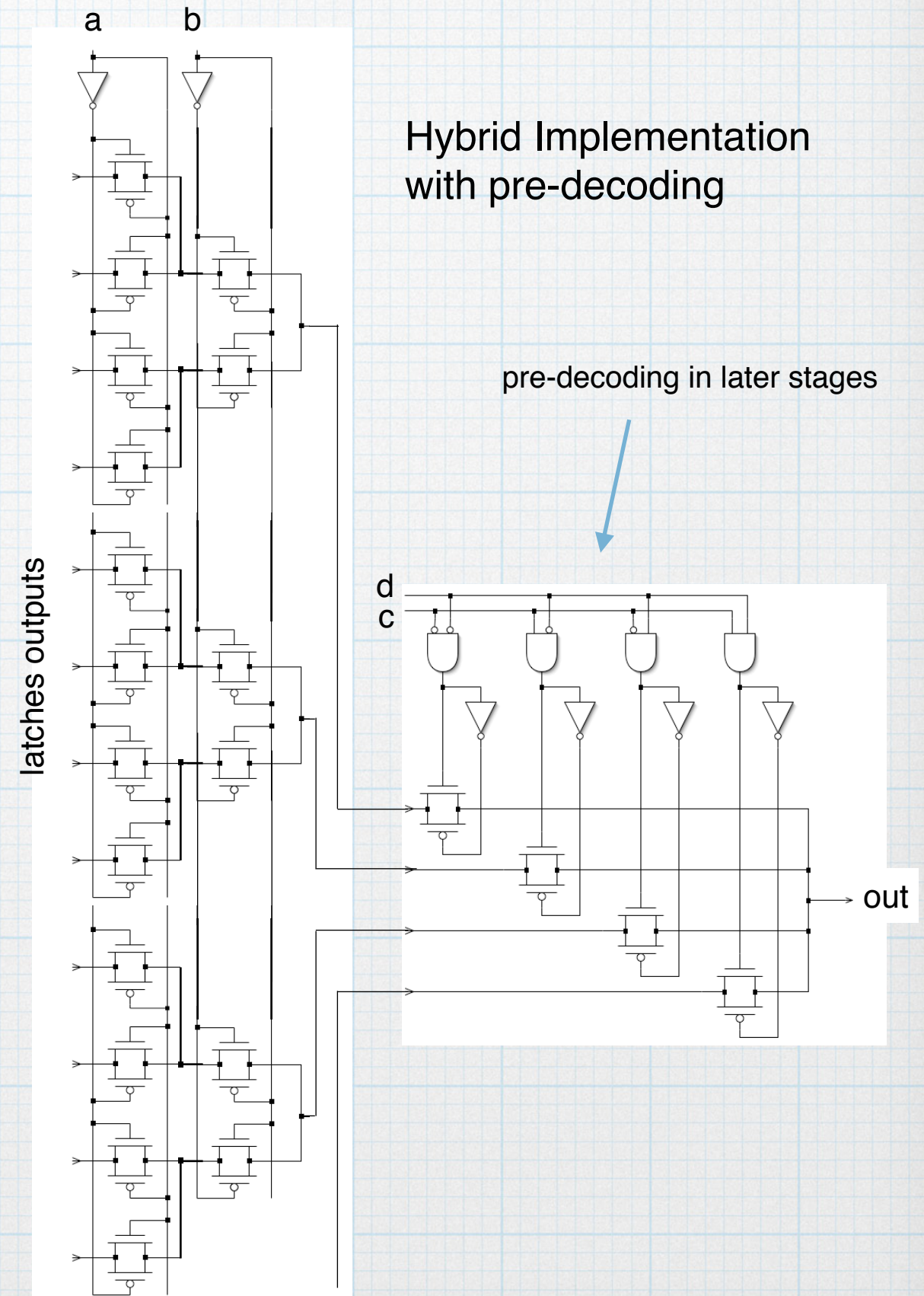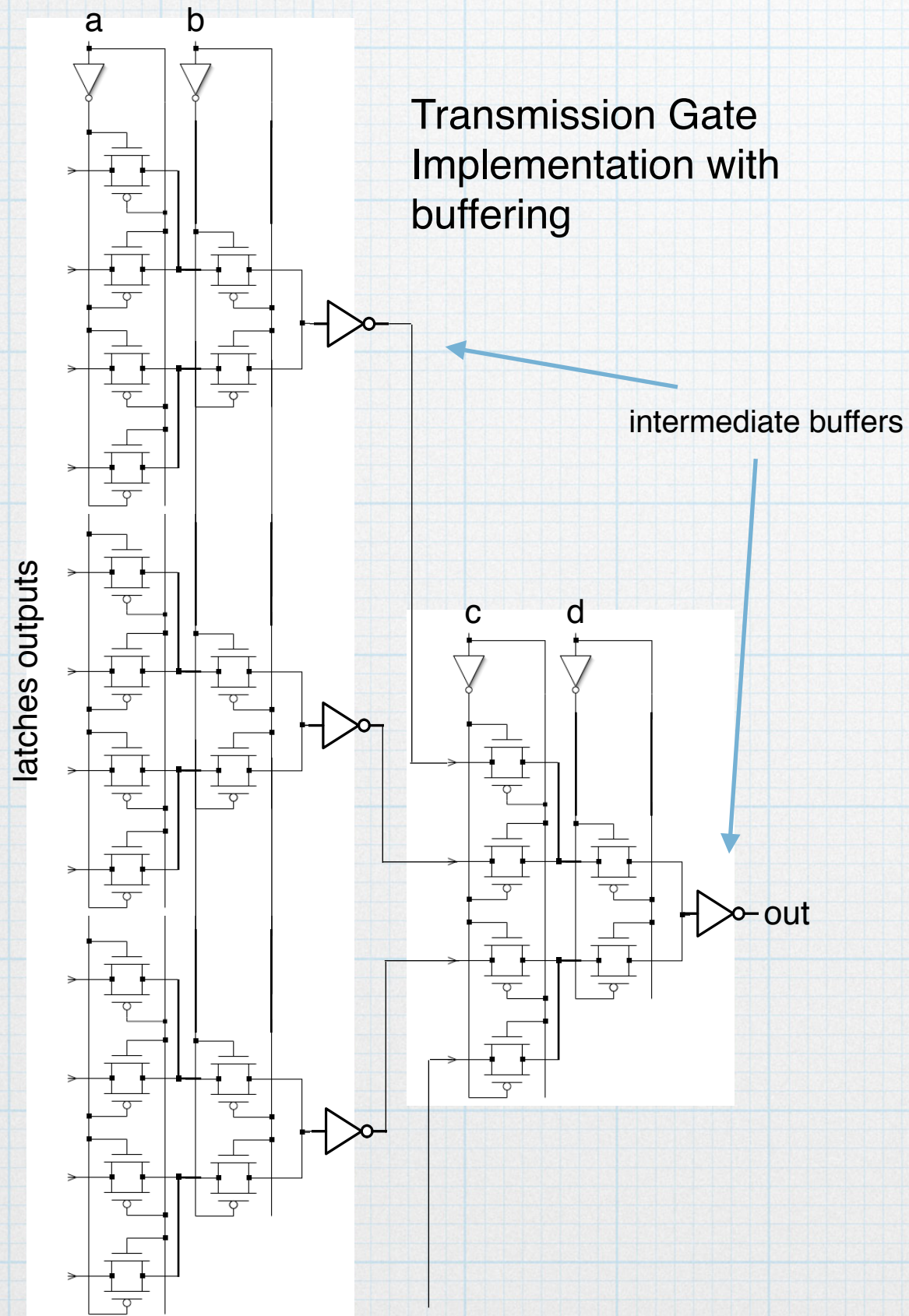

Large Mux layout considerations

- ▶ 4-to-1 example
- ▶ p-path & n-path for all a,b combinations

separately group p's and n's

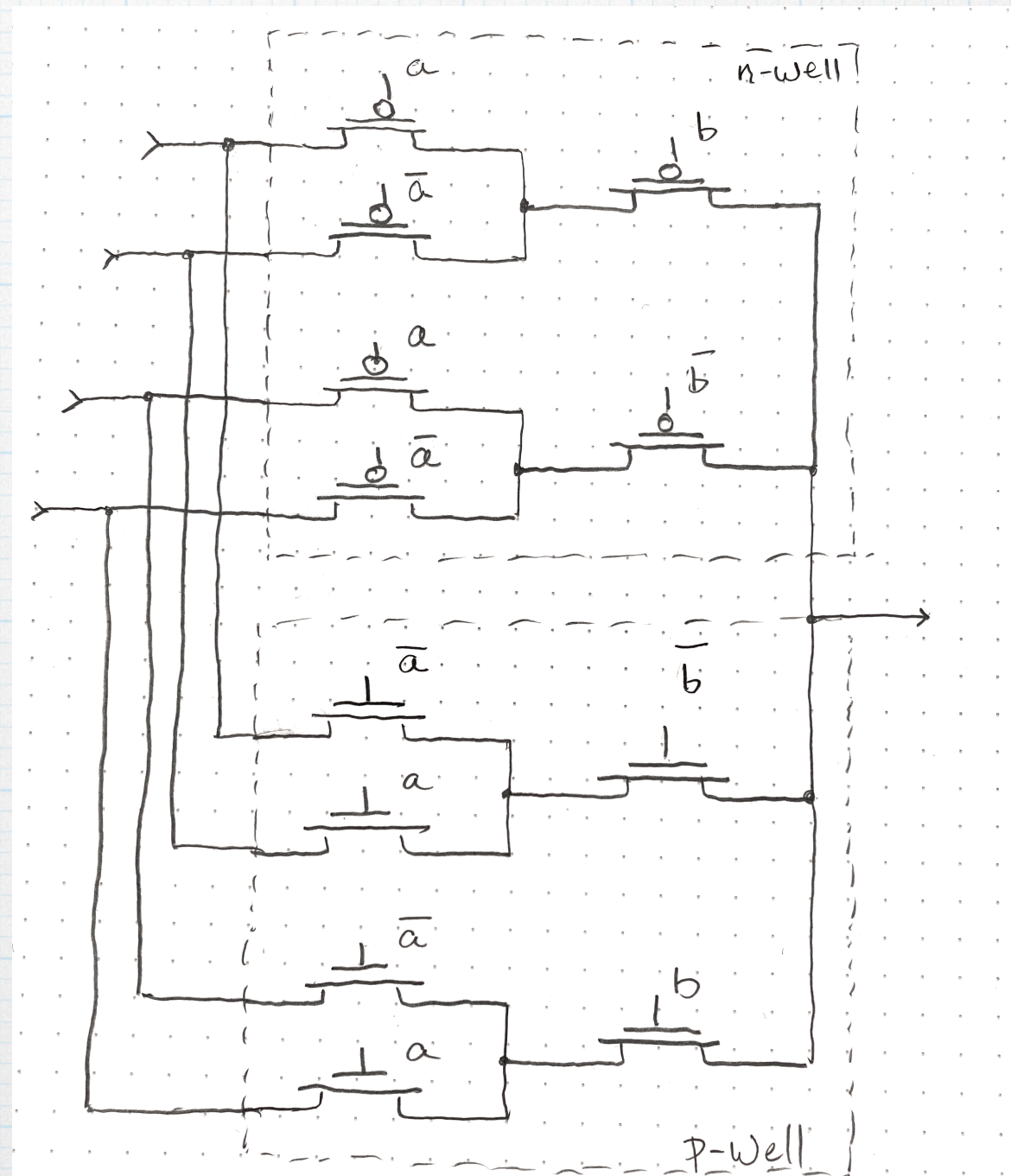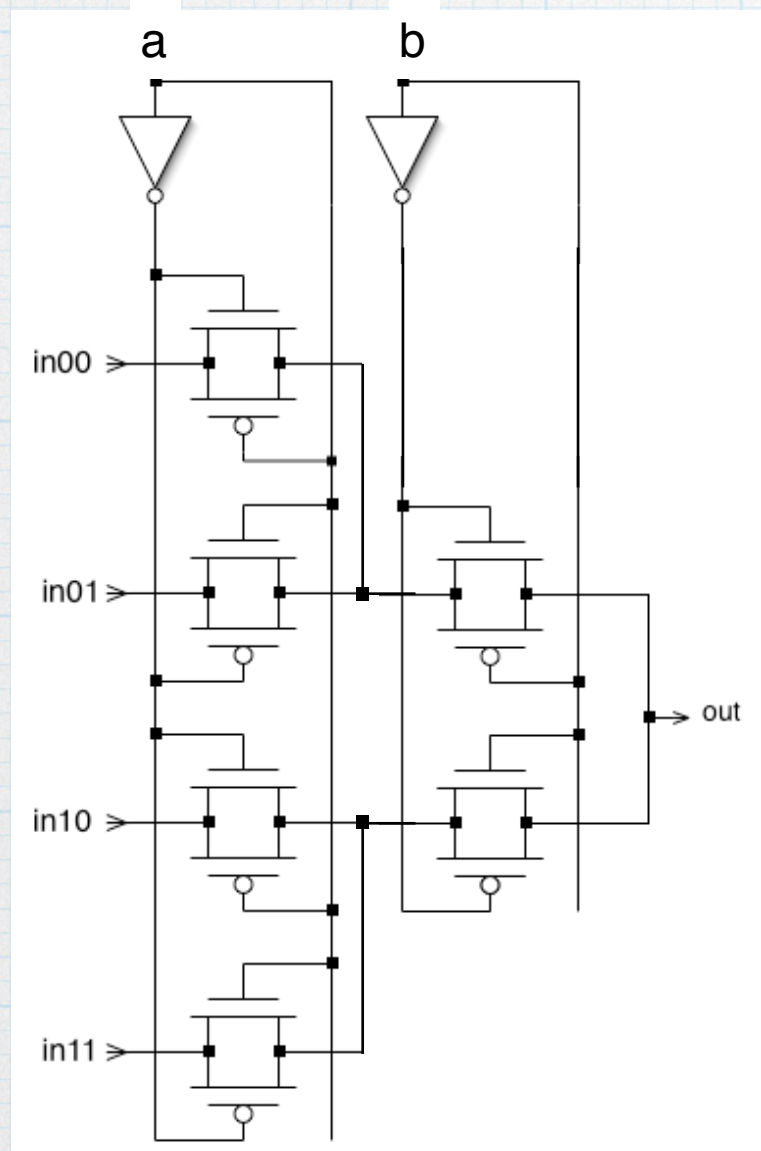

End of Lecture 12