

VLSI Design EE 523 Spring 2025

Shahid Masud Lecture 4

Topics for lecture 4



Simple working models for NMOS and PMOS as switch

Quiz Next week

- Pass Transistor Logic using simple CMOS models
 - Difference between restoring and non restoring logic
- Making 2:1 MUX using pass transistor logic
- Design of a CMOS Tri-state inverter
- Make a D-Latch using pass transistor logic
- Concept of Resistivity and Sheet Resistance in CMOS process
- Concept of Area Capacitance and square Capacitance in CMOS process
- Introducing MOS transistor theory applying voltages at gate, drain, source and bulk terminals and observe different effects and regions

Reading and Book



- Textbook can be downloaded online "CMOS VLSI Design by Weste and Harris, 4th Edition"
- Readings from Chapter 1, starting portion of Chapter 2
- For quiz, prepare from chapter 1 and lecture notes